

Magma

Pat Hanrahan

**CS448H: Agile Hardware Design
Winter 2017**

Verilog

Combinational logic: and4.v, andn4.v

Sequential logic: dff.v, tff.v

Procedural assignment: dffr.v

Combinational logic: always_comb1.v

Latch inference: latch.v, inferred.v

Blocking: qqblocking.v

Nonblocking: qqnonblocking.v

Combinational always: always_comb2.v

Race conditions: race*.v

Operator Type	Operator Symbol	Operation Performed	Number of Operands
Arithmetic	*	Multiply	2
	/	Divide	2
	+	Add	2
	-	Subtract	2
	%	Modulus	2
Logical	!	Logical negation	1
	&&	Logical and	2
		Logical or	2
Rational	>	Greater than	2
	<	Less than	2
	>=	Greater than or equal	2
	<=	Less than or equal	2
Equality	==	Equality	2
	!=	Inequality	2
	===	Case equality	2
	!==	Case inequality	2
Bitwise	~	Bitwise negation	1
	&	Bitwise and	2
		Bitwise or	2
	^	Bitwise xor	2
	^~ or ~^	Bitwise xnor	2
Reduction	&	Reduction and	1
	~&	Reduction nand	1
		Reduction or	1
	~	Reduction nor	1
	^	Reduction xor	1
	^~ or ~^	Reduction xnor	1
Shift	>>	Right shift	2
	<<	Left shift	2
Concatenation	{ }	Concatenation	any
Replication	{ { } }	Replication	any
Conditional	? :	Conditional	3

Verilog

- 1. Variables in `always` blocks must always be declared as `reg`, but may or may not be a `reg`.**
 - `always @(*)` is combinational, i.e. lhs is not a `reg`, but beware of `reg` inference(!). Use blocking assignment (`=`)
 - `always @(posedge clk)` is sequential, i.e. lhs is a `reg`. Use nonblocking assignments (`<=`)
- 2. "Procedural assignment" inside an `always` block looks like C, but is not sequentially executed like C, since it runs in parallel.**
- 3. Allows multiple assignments to a wire or `reg`**

Verilog

- 1. Designed for simulation. "testbenches" used to test code.**
- 2. These parts do not generate hardware. E.g. for and while statements**
- 3. Easy to write programs that can't be synthesized (because sequential code can't be synthesized)**
- 4. Does not use modern PL concepts**
 - **Poor type system**
 - **Poor support for module and abstraction**
 - **Poor support for meta-programming**
 - **...**
- 5. Yet another programming language ...**

Meta-programming

```
wire [`N-1:0] fsum;  
wire [`N-1:0] facout;
```

```
FA fa(J1[0], J3[0], 1'b0, fsum[0],  
facout[0]);
```

```
genvar i;  
generate  
for (i = 1; i < `N ; i = i + 1) begin:add  
    FA fa(J1[i], J3[i], facout[i-1],  
fsum[i], facout[i]);  
end
```

```
assign D5 = facout[`N-1];
```




```
wire [`N-1:0] fsum;  
wire [`N-1:0] facout;
```

```
FA fa0(J1[0], J3[0], 1'b0,  
        fsum[0], facout[0]);
```

```
% for i in range(1,N):  
FA fa${i}(J1[${i}], J3[${i}], facout[${i-1}],  
          fsum[${i}], facout[${i}]);  
% endfor
```

```
assign D5 = facout[`N-1];
```

 

Magma

Python meta-programs Circuits

Multi-Stage Meta-Programming

build

meta
program

synth

place
route

bit
stream

make

cpp

map

par

bitgen

bake

magma

yosis

arachne

icepack

Combinational Logic

Circuit Abstraction

1. Instantiate circuits

```
lut4 = LUT4(I0&I1)
```

```
ff = DFF()
```

Circuits are "like" functions

Circuit Abstraction

2. Wire circuits to other circuits

Explicitly

```
wire(I, ff.I)  
wire(ff.0, 0)
```

Using function calls

```
ff(lut(I))
```

NB. Circuits can only be "called" once


```
// And4
```

```
lut4 = LUT4(I0&I1&I2&I3)
```

```
lut4(main.J1[0],  
      main.J1[1],  
      main.J1[2],  
      main.J1[3])
```

```
wire( lut4, main.D5 )
```

Full Adder

 

fulladder.py


```
main = icestick.main()

def and2(a, b):
    return And2()(a,b)

def or3(a,b,c):
    return Or3()(a,b,c)

def xor3(a,b,c):
    return Xor3()(a,b,c)

def FullAdder(a,b,c):
    S = xor3(a,b,c)
    C = or3(and2(a,b),and2(b,c),and2(c,a))
    return S, C

S, C = FullAdder(main.J1[0],main.J1[1],main.J1[2])

wire( S, main.D1 )
wire( C, main.D2 )
```

```
// fulladder.v
module main (input [2:0] J1, output D2, output D1);
wire inst0_0;
wire inst1_0;
wire inst2_0;
wire inst3_0;
wire inst4_0;
SB_LUT4 #(.LUT_INIT(16'h9696)) inst0
(.I0(J1[0]), .I1(J1[1]), .I2(J1[2]), .I3(1'b0), .O(inst0_0));
SB_LUT4 #(.LUT_INIT(16'h8888)) inst1
(.I0(J1[0]), .I1(J1[1]), .I2(1'b0), .I3(1'b0), .O(inst1_0));
SB_LUT4 #(.LUT_INIT(16'h8888)) inst2
(.I0(J1[1]), .I1(J1[2]), .I2(1'b0), .I3(1'b0), .O(inst2_0));
SB_LUT4 #(.LUT_INIT(16'h8888)) inst3
(.I0(J1[2]), .I1(J1[0]), .I2(1'b0), .I3(1'b0), .O(inst3_0));
SB_LUT4 #(.LUT_INIT(16'hFEFE)) inst4
(.I0(inst1_0), .I1(inst2_0), .I2(inst3_0), .I3(1'b0), .O(inst4_0));
assign D2 = inst4_0;
assign D1 = inst0_0;
endmodule
```

Magma Product Types

$T = \text{Bit} \mid \text{Array}(n, T) \mid \text{Tuple}(T_1, T_2, \dots, T_n)$

- **Recursive product type (not algebraic data type)**
- **All types have fixed size**

$\text{Array}(n, T)$


$\text{Tuple}(T_1, T_2, \dots, T_n)$

- **Calling these functions returns a type (class)**
- **Generalizes *higher-kinded* types**

Behavioral Specification

behavioral

Sequential Logic

 

Toggle Flip-Flop

Sequential Logic

1. Flip-flop/Register

- Circuit which has an input I , an output O , and internal state
- CLK and CE
- RESET and SET

2. Sequential logic

- Compute next value using combinational logic as a function of the inputs and the previous state (FF output)
- Wire next value to FF input
- Results in a cyclic graph of circuits

```
# create ff holding state first
```

```
ff = FF()
```

```
# lut computes the next state ...
```

```
lut = LUT2( I0^I1 )
```


```
lut(T, ff)
```

```
# lut computes the next state
```

```
ff(lut)
```

```
wire( ff, 0 )
```

```
# Implicit clock
```

 


add

counter



Mantle

 **Standard Low-Level Hardware Library
(think libc and libm, TTL 7400 / CMOS 4000)**



Mantle libc for hardware

**And, Or, Xor, ...
Add, Sub, ...
Mux,
Registers
Shift registers
Counters
Memories
...**