



Combinational Logic

Pat Hanrahan

**CS448H: Agile Hardware Design
Winter 2017**


logisim

Logic.circ

  


Logisim

Xor.circ

 


Logisim

Three Representations

 

→ Unique

 → Many formulas (sum of products, logic minimization)




IceStick


and2.v

xor2.v


Xor2 -> Mux2

 



Mux4

 

ice40

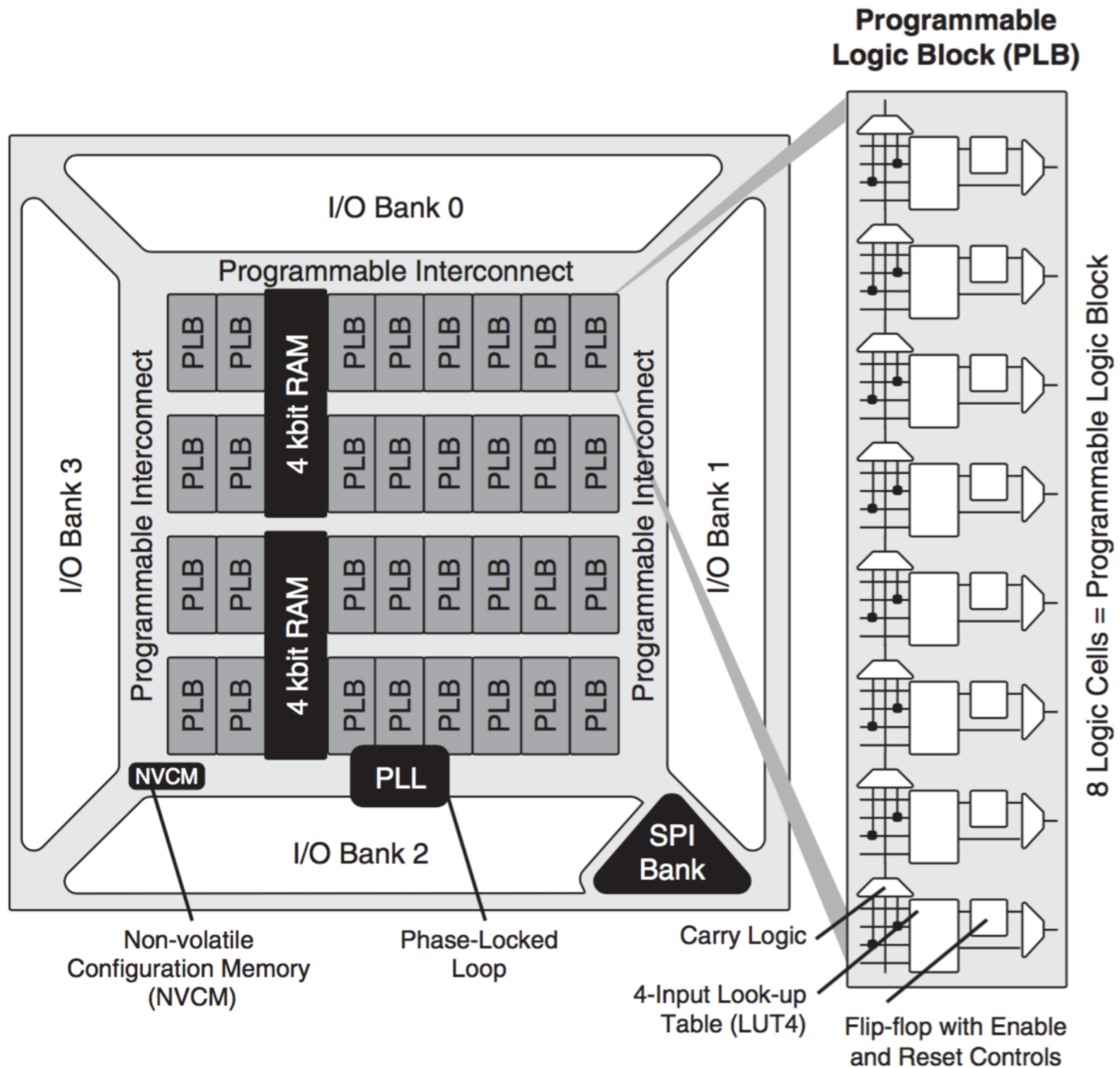

 

 

LUT4 has 16 entries

lut4.v
and2.v, or2.v, xor2.v


```
// Represent functions as bit patterns
```

```
// see lut.py
```

```
ZERO = 0b0000000000000000
```

```
ONE  = 0b1111111111111111
```

```
I0   = 0b1010101010101010
```

```
I1   = 0b1100110011001100
```

```
I2   = 0b1111000011110000
```

```
I3   = 0b1111111100000000
```

```
LUT4(ZERO)(i0,i1,i2,i3)==0
```

```
LUT4(ONE)(i0,i1,i2,i3)==1
```

```
LUT4(I0)(i0,i1,i2,i3)==i0
```

```
LUT4(I0^I1^I2^I3)(i0,i1,i2,i3)==i0^i1^i2^i3
```

```
LUT4((~I2&I0)|(I2&I1)(i0,i1,i2,i3)==i2?i1:i0
```

Combinational Functions

Logic


Arithmetic

Comparisons


Multiplexers

Decoders and Encoders


HalfAdder.circ

 

FullAdder.circ

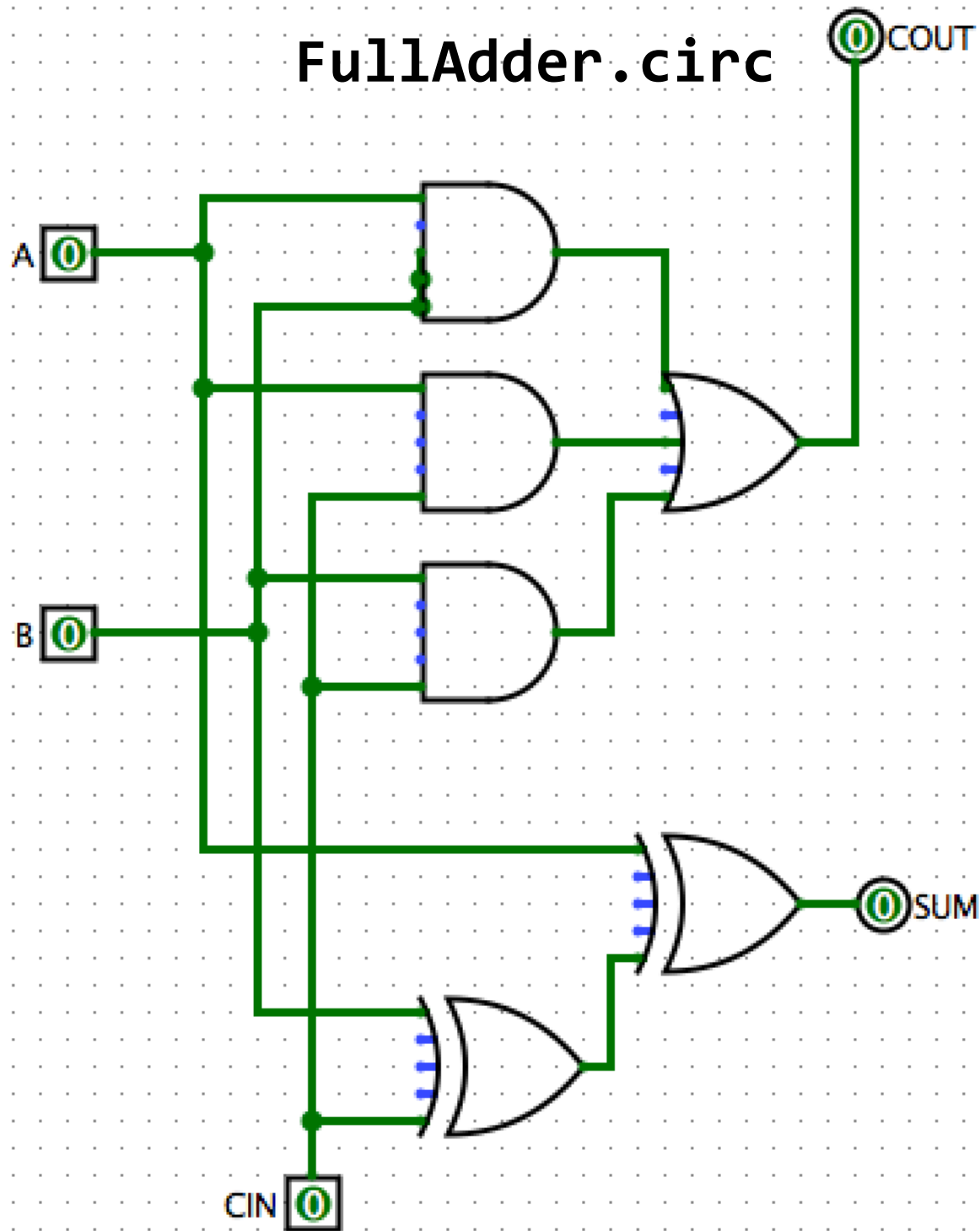

Add2.circ

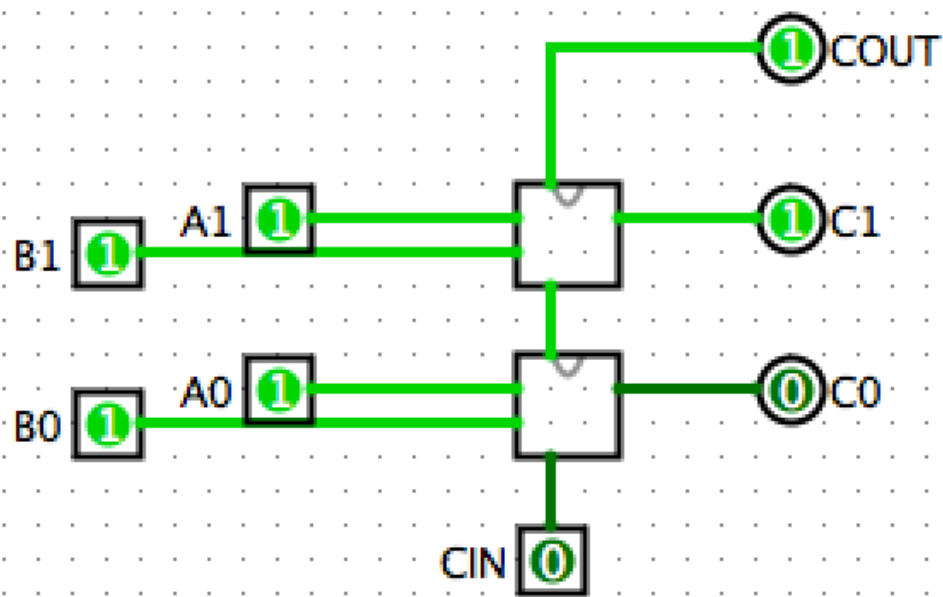

fa.v, add4.v

iceadd4.v

Combinational Logic

Combinational logic is an expression involving (combination of) logic gates

1. All gates should have valid inputs

2. No cycles

***Pure and total* function of inputs**

Executes continuously and in parallel



SR Flip Flop

