

# **Sequential Logic**

**Pat Hanrahan**

**CS448H: Agile Hardware Design  
Winter 2017**

# Combinational Logic

**Combinational logic is an expression involving (combination of) logic gates**

**1. All inputs connected to exactly one output**

**2. No cycles**

**Expression: Fixed topology and fixed data widths**

***Pure* and *total* function of inputs**

**Executes continuously and in parallel**

**// Truth table for Mux2**

<b>S</b>	<b>A</b>	<b>B</b>	<b>O</b>
----------	----------	----------	----------

<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
----------	----------	----------	----------

<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>
----------	----------	----------	----------

<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>
----------	----------	----------	----------

<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>
----------	----------	----------	----------

<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>
----------	----------	----------	----------

<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>
----------	----------	----------	----------

<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>
----------	----------	----------	----------

<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>
----------	----------	----------	----------

**// Truth table for Mux2 - Don't Care**

<b>S</b>	<b>A</b>	<b>B</b>	<b>O</b>
----------	----------	----------	----------

<b>0</b>	<b>0</b>	<b>X</b>	<b>0</b>
----------	----------	----------	----------

<b>0</b>	<b>0</b>	<b>X</b>	<b>0</b>
----------	----------	----------	----------

<b>0</b>	<b>1</b>	<b>X</b>	<b>1</b>
----------	----------	----------	----------

<b>0</b>	<b>1</b>	<b>X</b>	<b>1</b>
----------	----------	----------	----------

<b>1</b>	<b>X</b>	<b>0</b>	<b>0</b>
----------	----------	----------	----------

<b>1</b>	<b>X</b>	<b>1</b>	<b>1</b>
----------	----------	----------	----------

<b>1</b>	<b>X</b>	<b>0</b>	<b>0</b>
----------	----------	----------	----------

<b>1</b>	<b>X</b>	<b>1</b>	<b>1</b>
----------	----------	----------	----------

**// Truth table for Mux2 - Don't care**

<b>S</b>	<b>A</b>	<b>B</b>	<b>O</b>
----------	----------	----------	----------


<b>0</b>	<b>0</b>	<b>X</b>	<b>0</b>
----------	----------	----------	----------

<b>0</b>	<b>1</b>	<b>X</b>	<b>1</b>
----------	----------	----------	----------

<b>1</b>	<b>X</b>	<b>0</b>	<b>0</b>
----------	----------	----------	----------

<b>1</b>	<b>X</b>	<b>1</b>	<b>1</b>
----------	----------	----------	----------

## Add2.circ


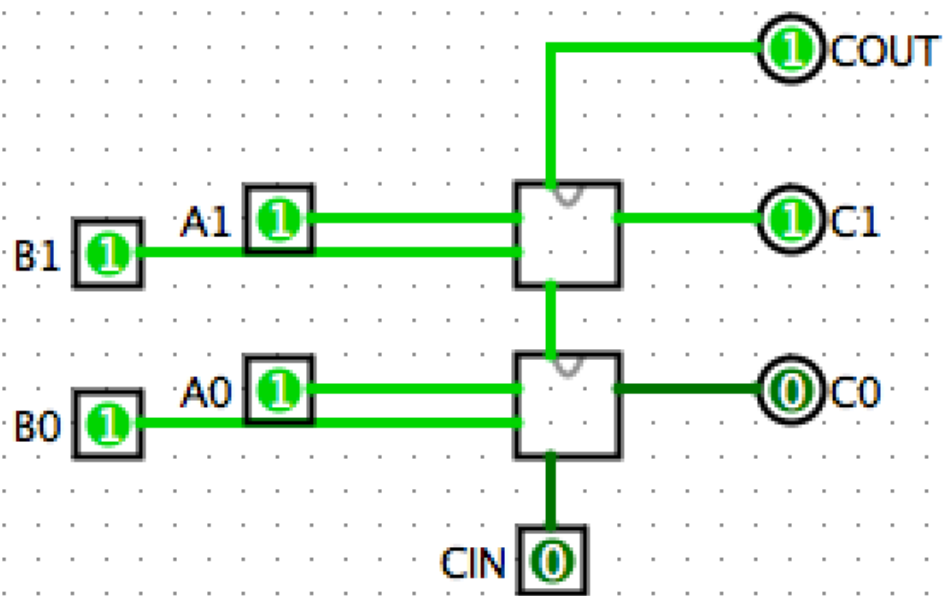




**iceadd4.v**





# HalfAdder.circ

 
 


**Assuming each gate has the same delay T**

# FullAdder.circ

 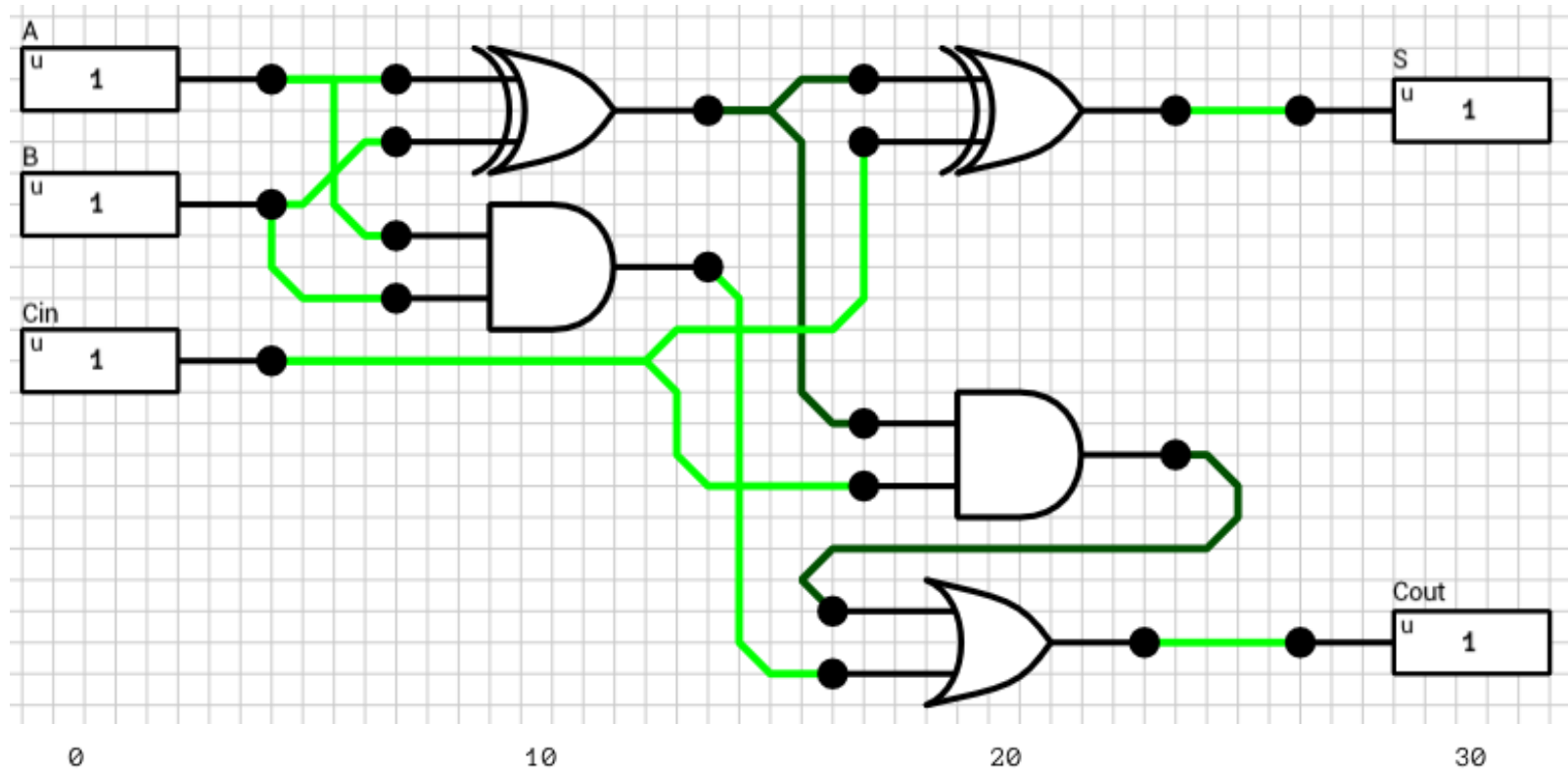


## Glitches!

 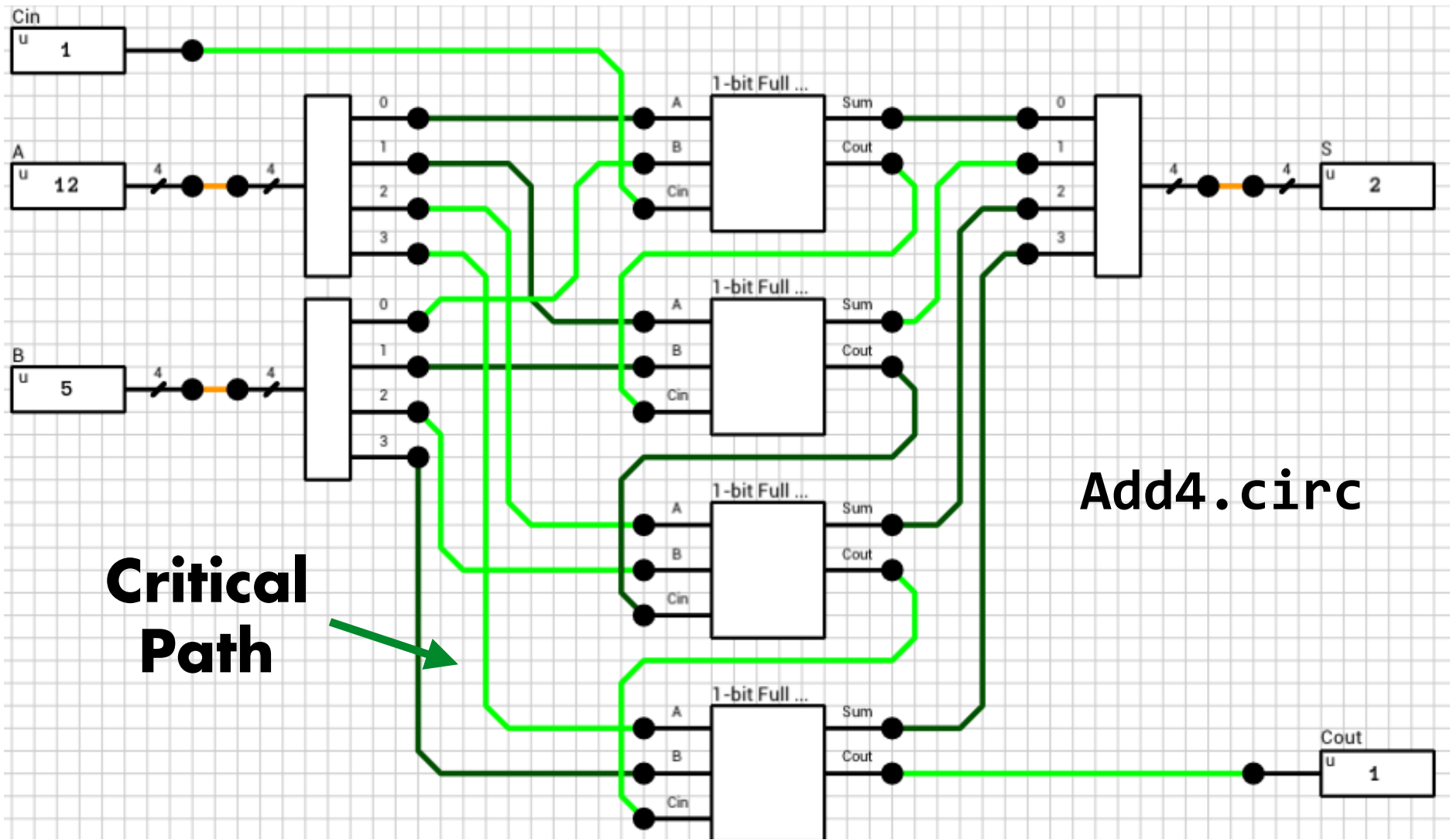

 
# Propagation Delay

**Need to wait for circuit  
to stabilize**  
**Critical path determines  
how long**  
**Timing analysis**



**iceaddn.v timing analysis**


# SR Flip Flop

 

# D Flip Flop



# D Flip Flop (DFF)

 


$\overline{\text{SET}}$	$\overline{\text{RESET}}$	D	CK	Q	$\overline{\text{Q}}$
0	1	-	-	1	0
1	0	-	-	0	1
0	0	-	-	1	1
1	1	1	$\downarrow$	1	0
1	1	0	$\downarrow$	0	1

- Has an input D, outputs Q and /Q, and internal state
- CLK (rising) and CE (clock enable)
- RESET and SET (synchronous/asynchronous)



# Sequential Logic

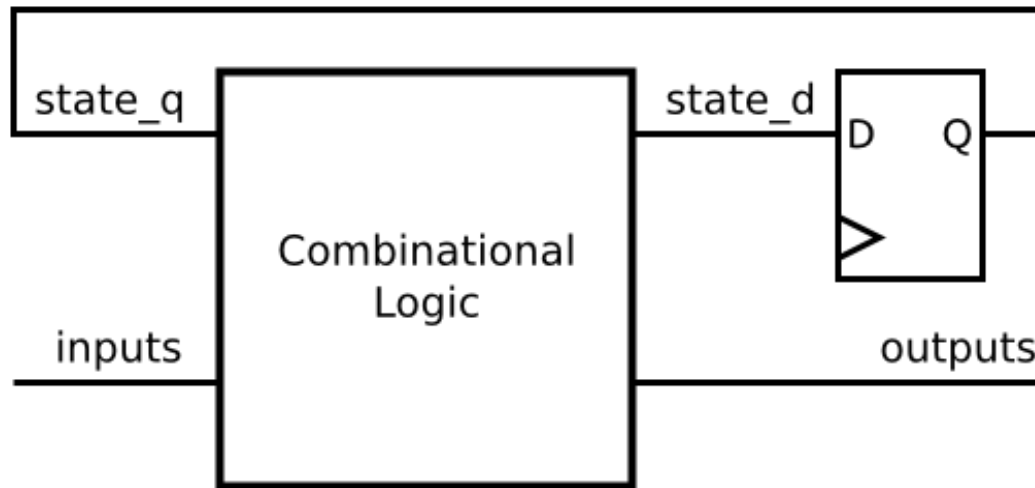

## Finite State Machine

# **Sequential Logic**

**All flip flops share a global, synchronous clock**


**All Flip flops change state simultaneously on the rising edge of the clock**

**Flip flops can be conditionally updated based on the clock enable**


**The new value is a combination function of the inputs and the values currently stored in the flip flop**

**Outputs are combinational functions of the flip flops and the inputs**

# T (toggle) Flip Flop

 

# TFF

 


**tff.v**

## Table of Contents

Register Primitives .....	6
SB_DFF .....	6
SB_DFFE .....	8
SB_DFFSR .....	10
SB_DFFR .....	12
SB_DFFSS .....	14
SB_DFFS .....	16
SB_DFFESR .....	18
SB_DFFER .....	20
SB_DFFESS .....	22
SB_DFFES .....	24
SB_DFFN .....	26
SB_DFFNE .....	28
SB_DFFNSR .....	30
SB_DFFNR .....	32
SB_DFFNSS .....	34
SB_DFFNS .....	36
SB_DFFNESR .....	38
SB_DFFNER .....	40
SB_DFFNESS .....	42
SB_DFFNES .....	44
 
## D Flip-Flop

Data: D is loaded into the flip-flop during a rising clock edge transition.



Inputs			Output
	D	C	Q
	0		0
	1		1
Power on State	X	X	0

Key

- Rising Edge
- 1 High logic level
- 0 Low logic level
- X Don't care
- ? Unknown

## HDL use

This register is inferred during synthesis and can also be explicitly instantiated.

## Verilog Instantiation


// SB\_DFF - D Flip-Flop.

```
SB_DFF SB_DFF_inst (  
    .Q(Q),           // Registered Output  
    .C(C),           // Clock  
    .D(D),           // Data  
);
```


**counter.v**



# Shift Register

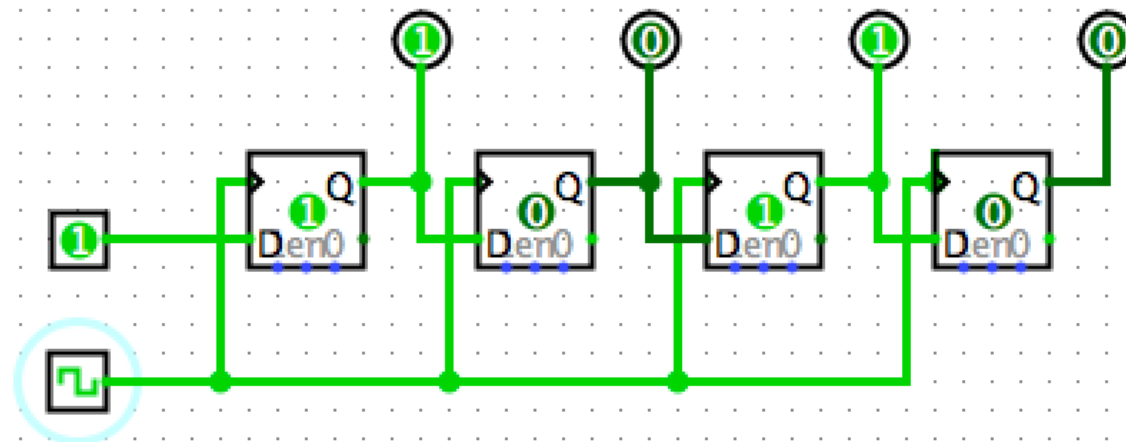

# Johnson or Twisted Ring Counter

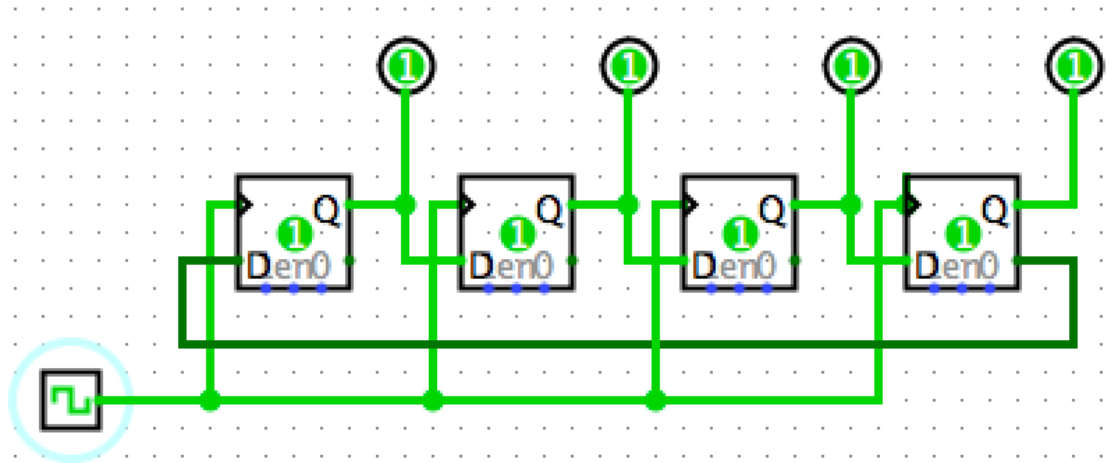

Logisim: Log main of Johnson

Selection Table File

Output(340,190)	Output(420,190)	Output(500,190)	Output(580,190)
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1

Close Window

# Assignment 1

## Hardware

- Icestick

## Software

- yosys
- arachne
- icestorm

**Due Fri Jan 27th at 12 midnight**