Sequential Logic

Pat Hanrahan

CS448H: Agile Hardware Design Winter 2017

Combinational Logic

Combinational logic is an expression involving (combination of) logic gates

- 1. All inputs connected to exactly one output
- 2. No cycles

Expression: Fixed topology and fixed data widths

Pure and total function of inputs


Executes continuously and in parallel

```
// Truth table for Mux2
S A B O
0000
0 0 1 0
0 1 0 1
0 1 1 1
1000
1 0 1 1
1 1 0 0
1 1 1 1
```


```
// Truth table for Mux2 - Don't Care
SABO
0 0 X 0
0 0 X 0
0 1 X 1
0 1 X 1
1 X 0 0
1 X 1 1
1 X 0 0
1 X 1 1
```

```
// Truth table for Mux2 - Don't care
S A B O
0 0 X 0
0 1 X 1
1 X 0 0
1 X 1 1
```

Add2.circ

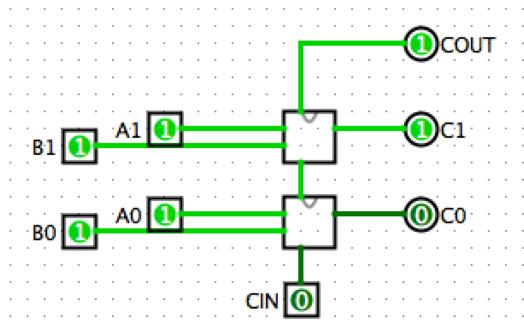



Shared Block-Level Controls

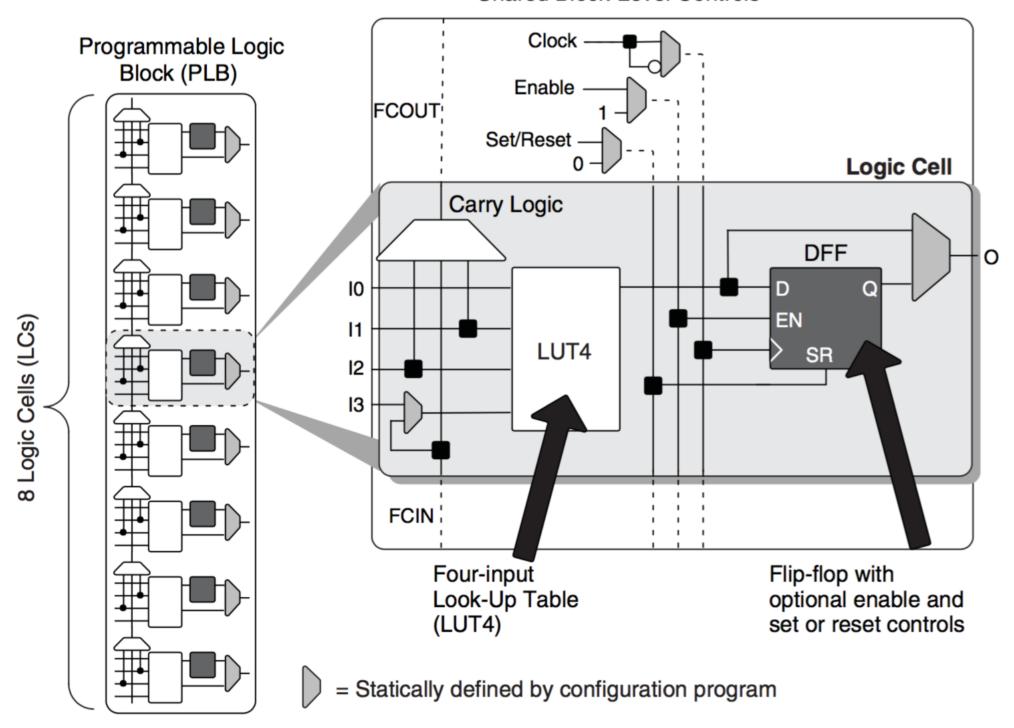

iceadd2.v

HalfAdder.circ

 


 

Assuming each gate has the same delay T


http://dls.makingartstudios.com/tags/adders/index.html

FullAdder.circ

 


Glitches!

 http://dls.makingartstudios.com/tags/adders/index.html



http://dls.makingartstudios.com/tags/adders/index.html


Glitches!

 


Propagation Delay

Need to wait for circuit to stabilize Critical path determines how long Timing analysis iceaddn.v timing analysis

SR Flip Flop

 

D Flip Flop

 

D Flip Flop (DFF)

Q


1

0

CK

Q

1

 

- Has an input D, outputs Q and /Q, and internal state
- CLK (rising) and CE (clock enable)
- RESET and SET (synchronous/asynchronous)

Sequential Logic

All flip flops share a global, synchronous clock


All Flip flops change state simultaneously on the rising edge of the clock

Flip flops can be conditionally updated based on the clock enable


The new value is a combination function of the inputs and the values currently stored in the flip flop

Outputs are combinational functions of the flip flops and the inputs

T (toggle) Flip Flop

 

TFF

 


tff.v

Table of Contents

Register Primitives	6
SB_DFF	6
SB_DFFE	
SB_DFFSR	10
SB_DFFR	12
SB_DFFSS	14
SB_DFFS	16
SB_DFFESR	18
SB_DFFER	20
SB_DFFESS	22
SB_DFFES	24
SB_DFFN	26
SB_DFFNE	28
SB_DFFNSR	30
SB_DFFNR	32
SB_DFFNSS	34
SB_DFFNS	36
SB_DFFNESR	38
SB_DFFNER	40
SB_DFFNESS	42
SB_DFFNES	44

D Flip-Flop

 Data: D is loaded into the flip-flop during a rising clock edge transition.



Inputs		Output	
	D	С	Q
	0	1	0
	1	1	1
Power on State	Х	X	0

Key

✓ Rising Edge

1 High logic level

0 Low logic level

X Don't care

? Unknown


HDL use

This register is inferred during synthesis and can also be explicitly instantiated.


Verilog Instantiation


counter.v

Shift Register

 


Johnson or Twisted Ring Counter

 

 

Sequential Logic

 

Finite State Machine

Assignment 1

Hardware

■ Icestick

Software

- **■** yosys
- arachne
- **■** icestorm

Due Fri Jan 27th at 12 midnight