


Pico40 Processor

Variation on a Theme by Ken Chapman

Pat Hanrahan

**CS448H: Agile Hardware Design
Winter 2017**

Pico40

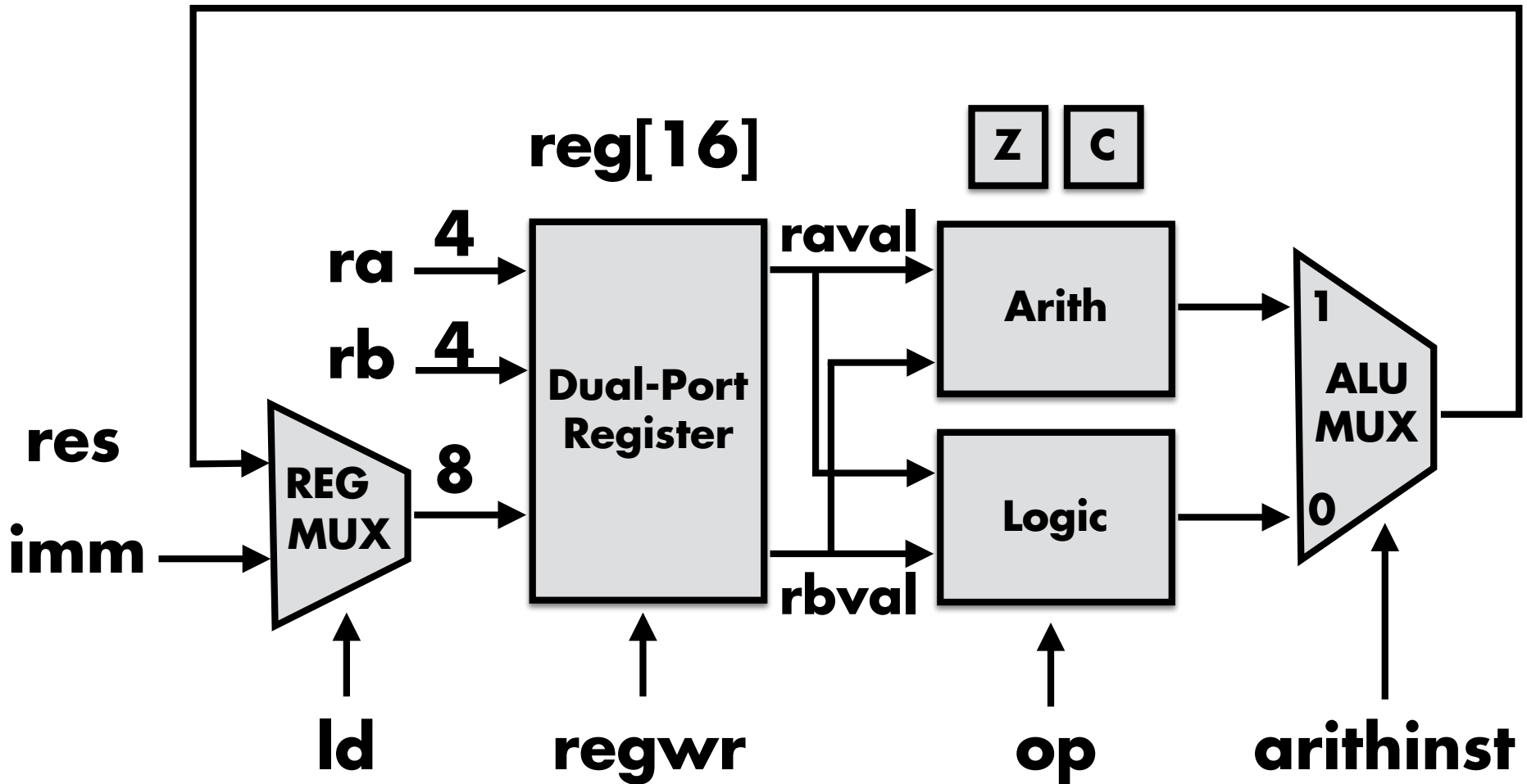

0000aaaabbbb0000	"mov"
0001aaaabbbb0000	"and_"
0010aaaabbbb0000	"or_"
0011aaaabbbb0000	"xor"

0100aaaabbbb0000	"add"
0101aaaabbbb0000	"sub"
0110aaaabbbb0000	"adc"
0111aaaabbbb0000	"sbc"

1000aaaaiiiiiiii	"ldlo"
1001aaaaiiiiiiii	"ldhi"
1010aaaaiiiiiiii	"ld"
1011aaaaiiiiiiii	"st"

1100cccciiiiiiii	"jmpc"
1101cccciiiiiiii	"callc"
1110cccc00000000	"retc"

```
from tiny import *
```

```
def mov ( a, b ):  
    a = checku ( a , 4 )  
    b = checku ( b , 4 )  
    emit( 0x0 | (a<<8) | (b<<4) )
```

```
def and_ ( a, b ):  
    a = checku ( a , 4 )  
    b = checku ( b , 4 )  
    emit( 0x1000 | (a<<8) | (b<<4) )
```

```
def or_ ( a, b ):  
    a = checku ( a , 4 )  
    b = checku ( b , 4 )  
    emit( 0x2000 | (a<<8) | (b<<4) )
```

```
def xor ( a, b ):  
    a = checku ( a , 4 )  
    b = checku ( b , 4 )  
    emit( 0x3000 | (a<<8) | (b<<4) )
```


```
from pico import *
```


```
def prog():  
    ldlo(r0,0)  
    ldlo(r1,1)  
    loop = label()  
    add(r0,r1)  
    st(r0, 0)  
    jmp(loop)
```

```
mem = assemble(prog)
```

```
save(mem, 'a.mem') // Show a.mem
```

RAMB

 

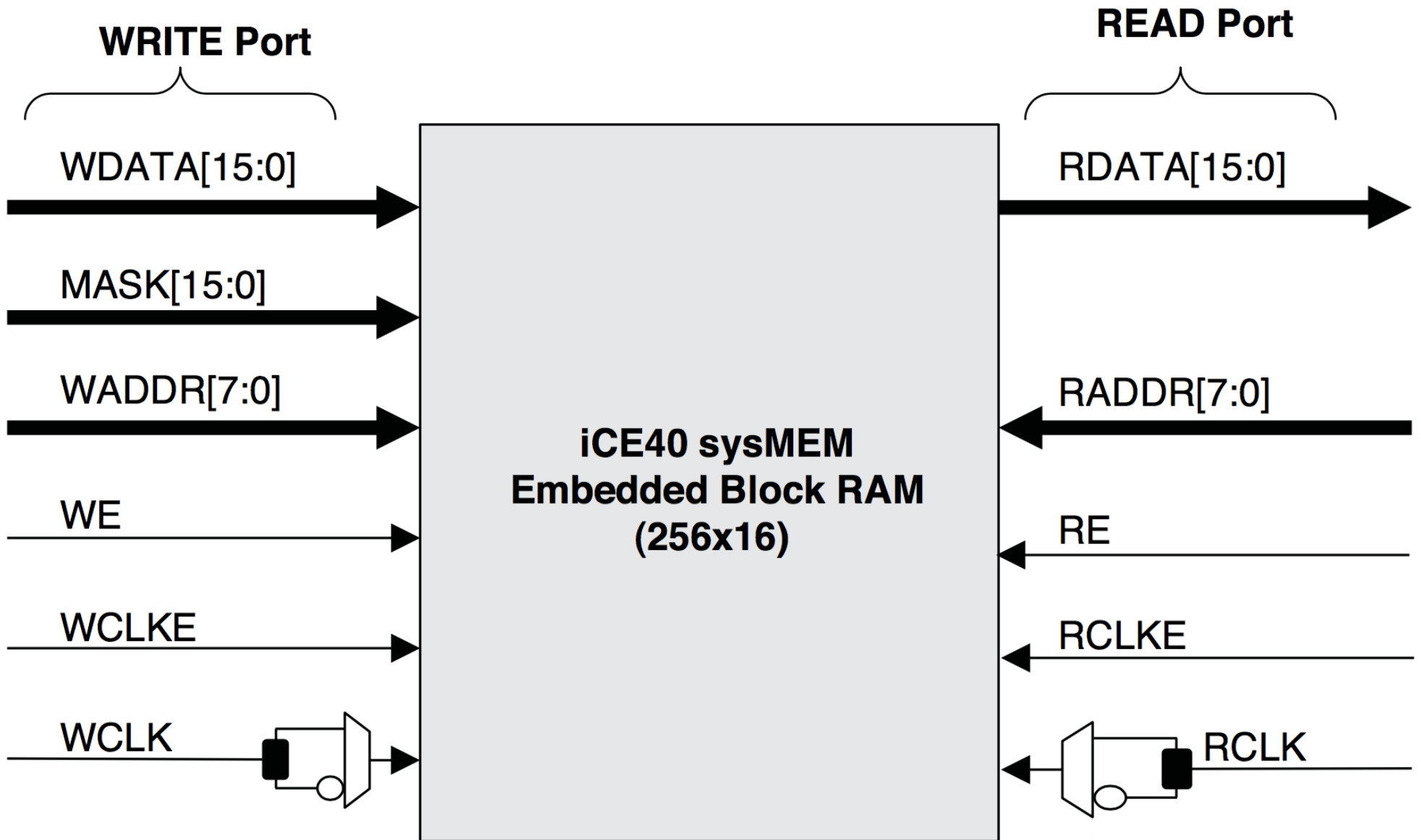

ADDRN, INSTN, N = 8, 16, 8

mem = readmem('a.mem', 1<<ADDRN)

initialize program memory

romb = ROMB(mem))

inst = romb.RDATA

instruction decode

addr = inst[0:ADDRN]

imm = inst[0:N]

rb = inst[4:8]


ra = inst[8:12]

cc = inst[8:12]

op = inst[12:14]


insttype = inst[14:16]

Sequencer

 

```
def Sequencer(n):  
    pc = Register(n, ce=True)  
    add = Add(n)  
    add( pc, constarray(1,n) )  
    mux = Mux(2, n)  
    wire(add.0, mux.I0)  
    pc(mux)  
  
    return AnonymousCircuit("addr", mux.I1  
                             "jump", mux.S,  
                             "we",    pc.CE,  
                             "0",    pc.0)
```


Figure 16-3. EBR Module Timing Diagram¹

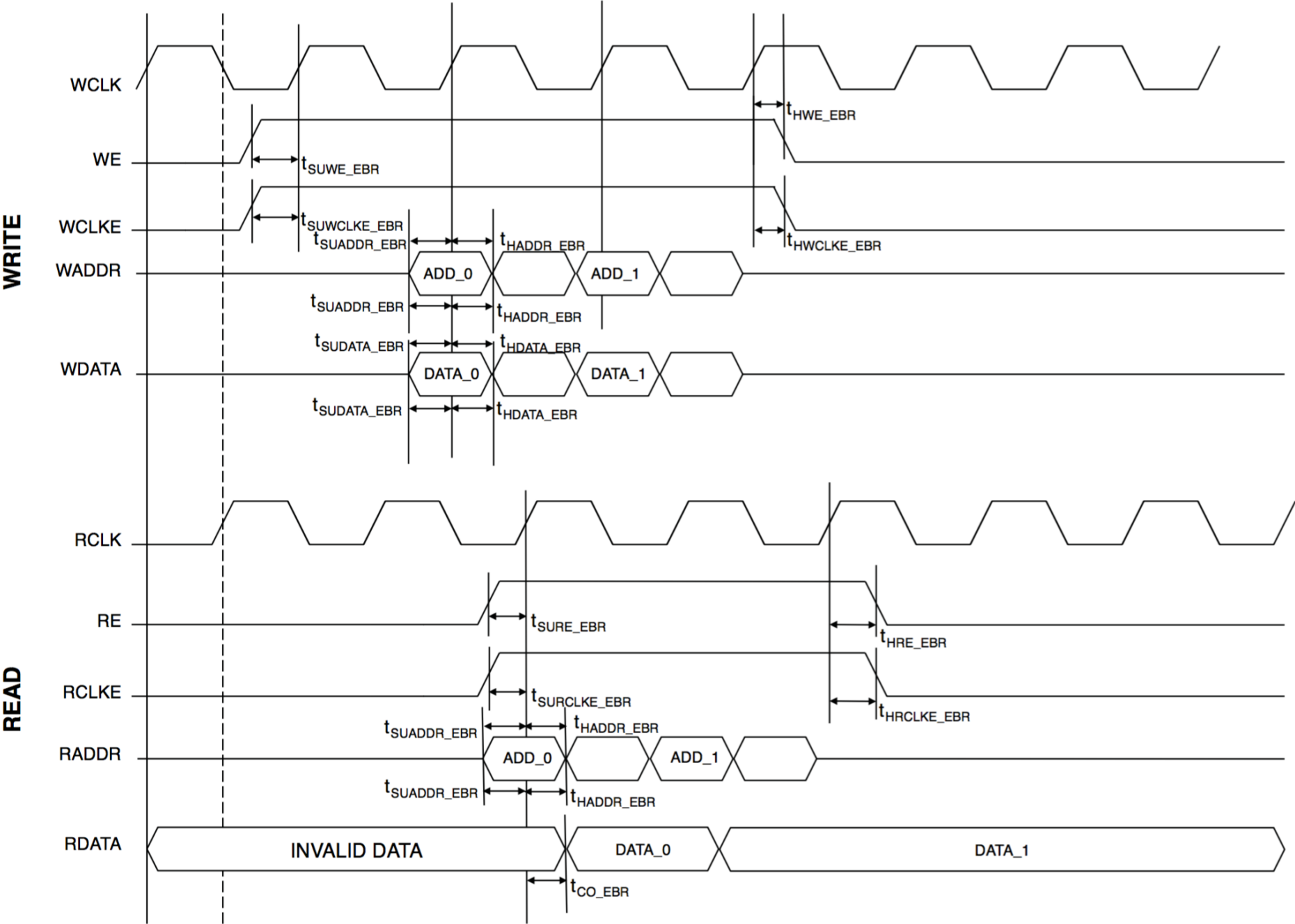

RADDR=pc


inst=RAMB[RADDR]

phase

 


↑
fetch


↑
decode
execute

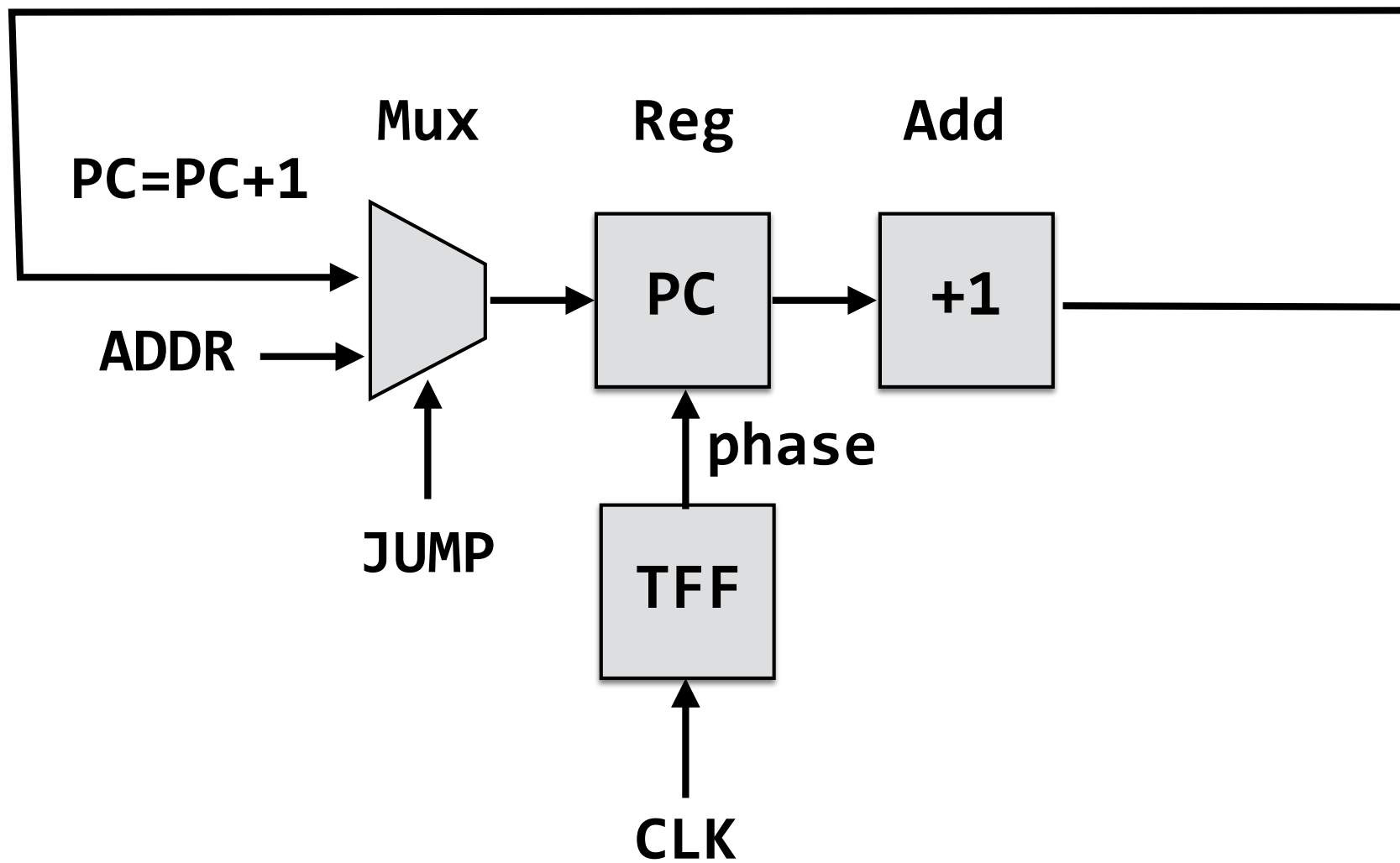

alu.py

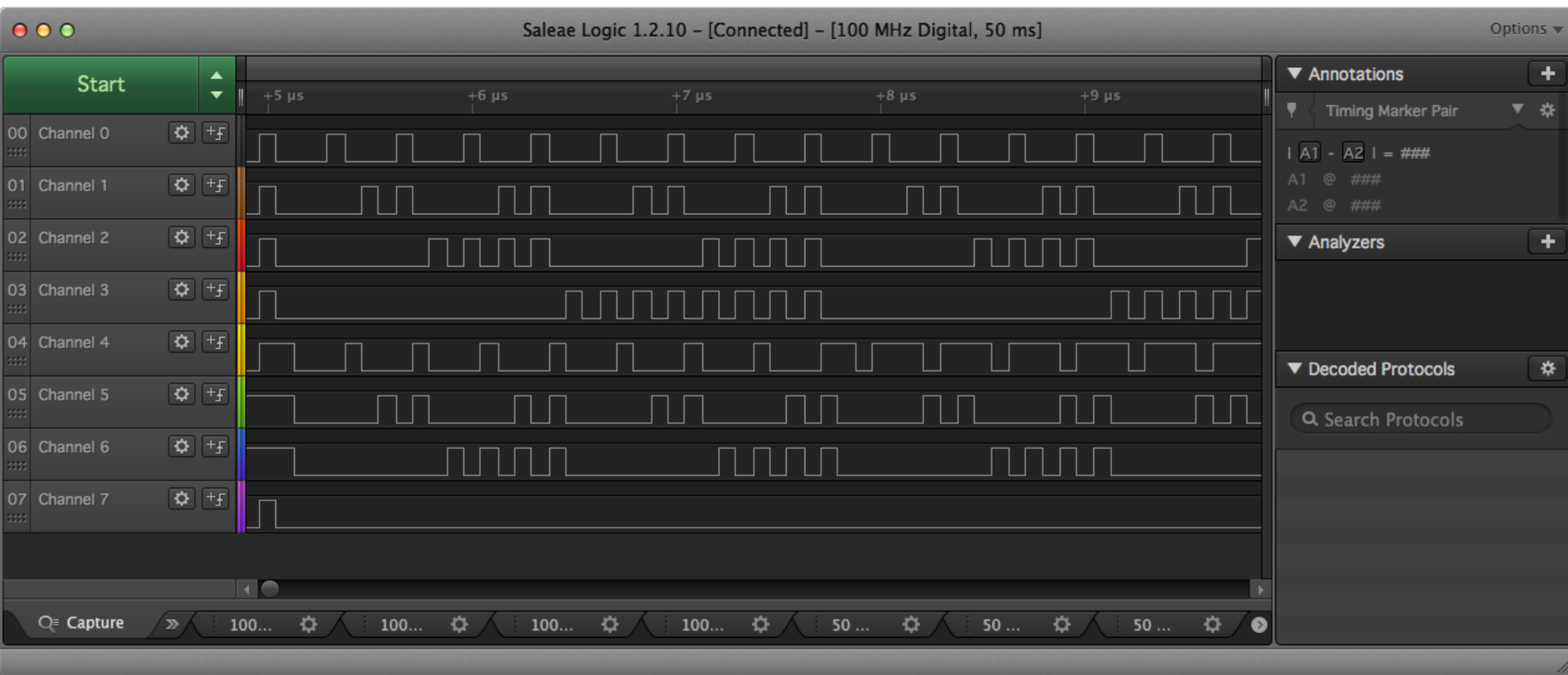


jmp.py

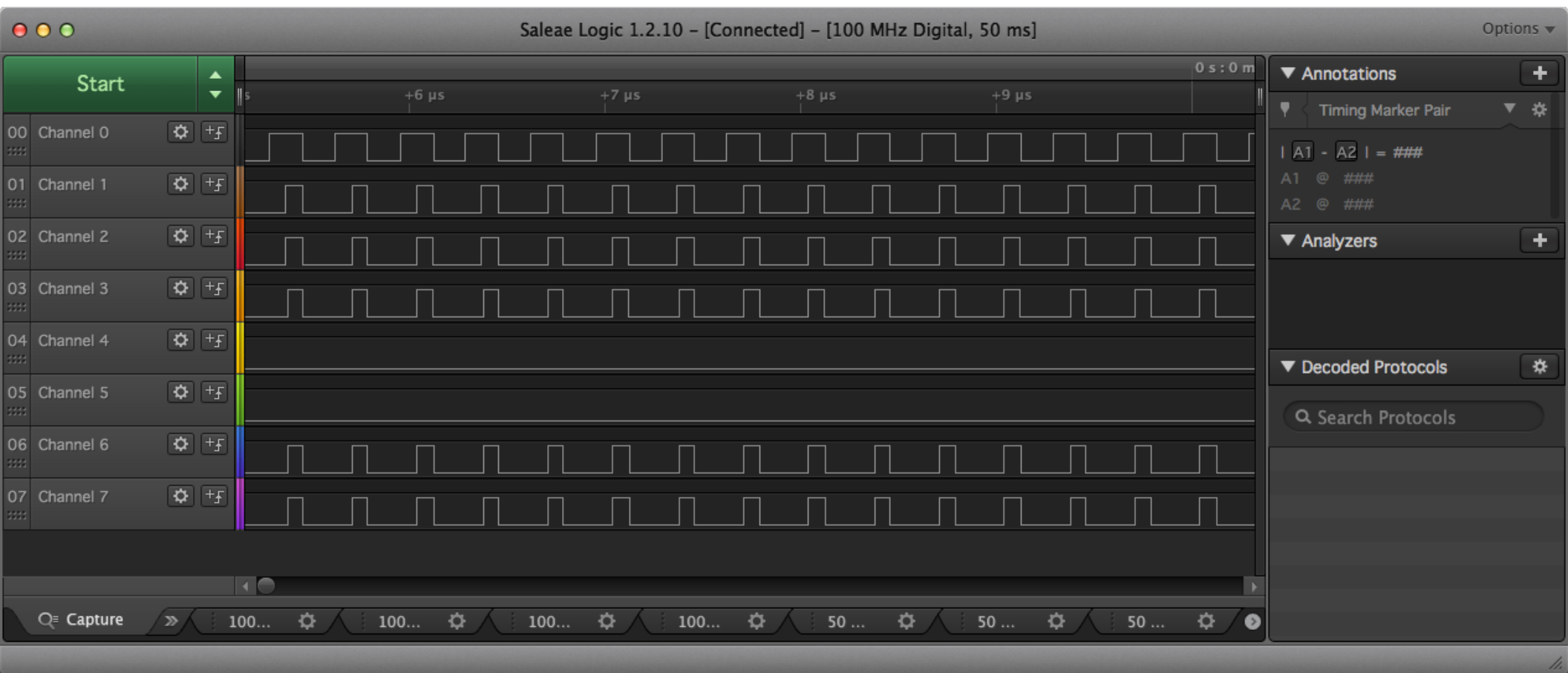


Dual-Ported Registers

`ram.py`

ldlo.py (show pc and inst)

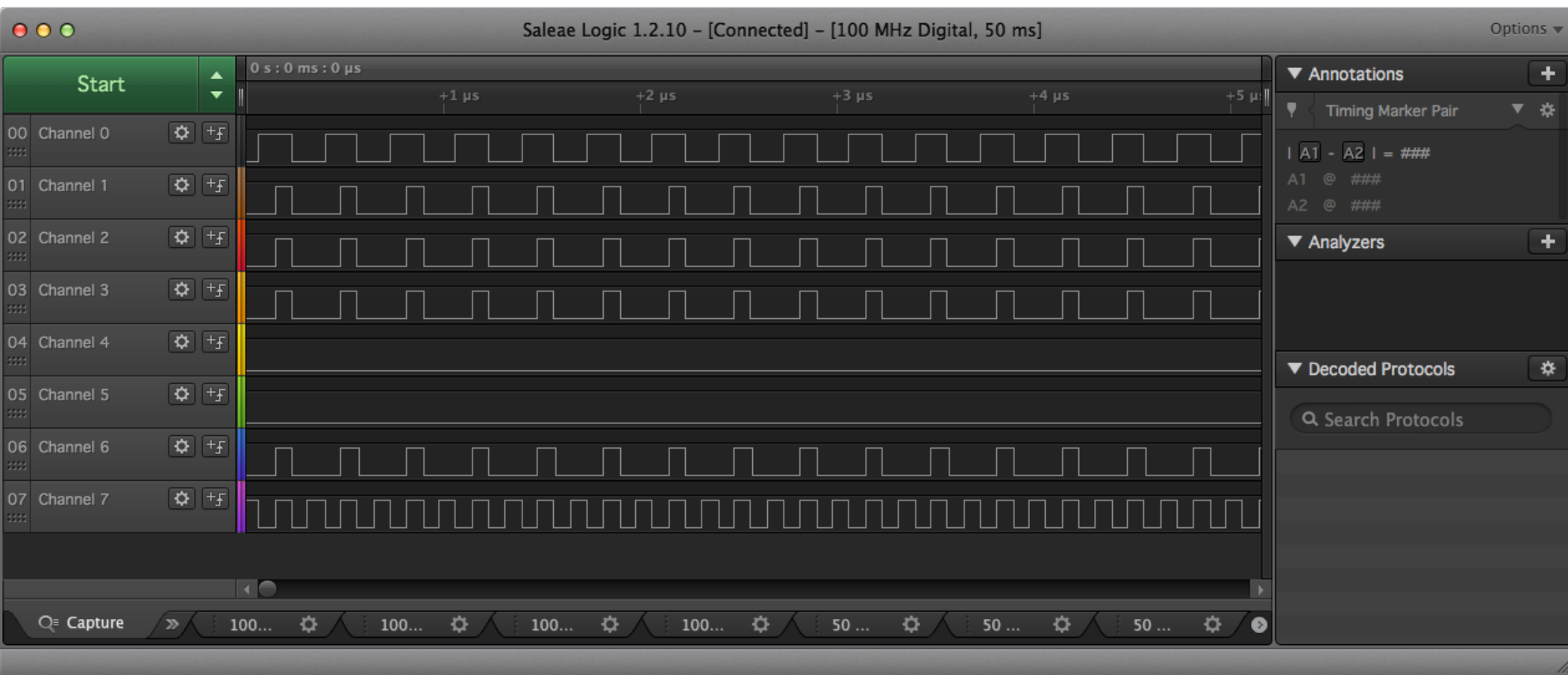


ldlo.py (show pc and res)

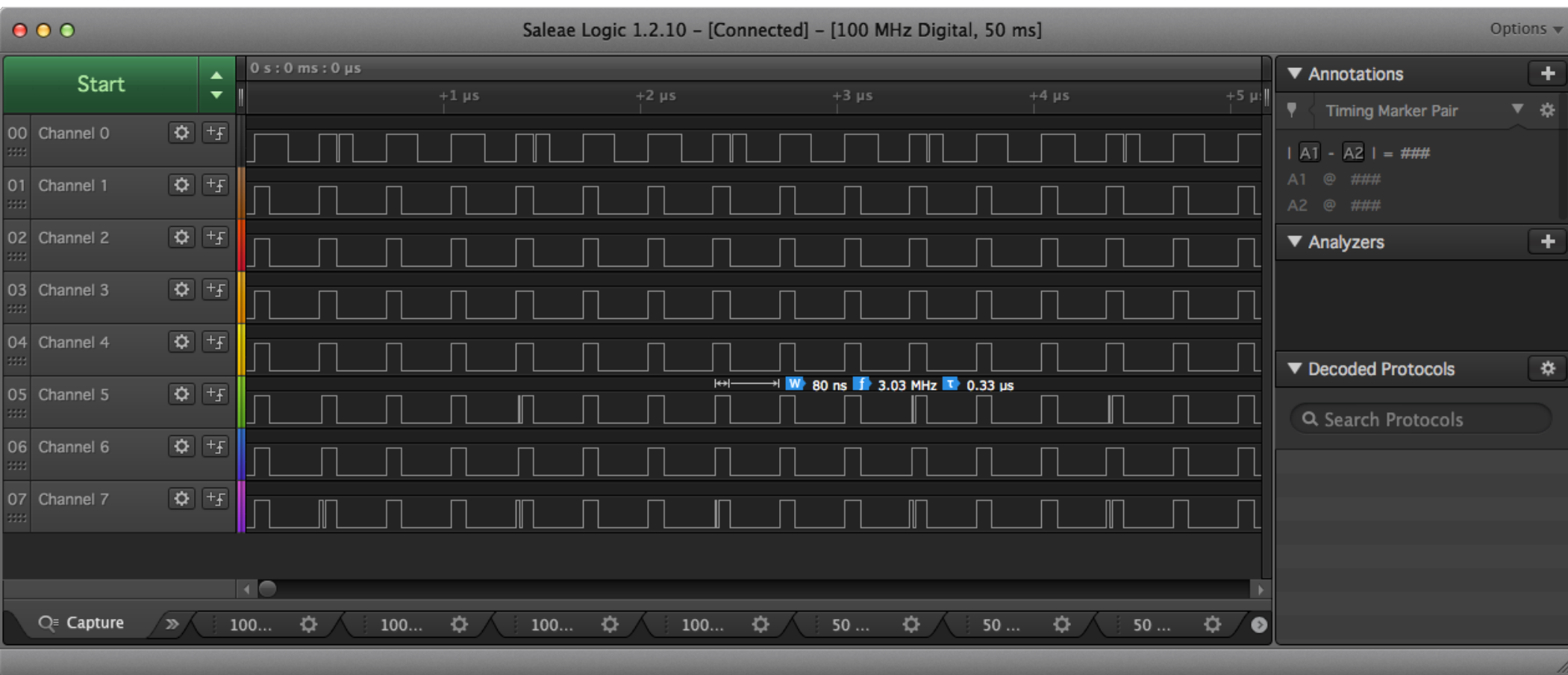


Note glitches!

Logic Unit

Logic Unit

 

Logical Group					
I3	I2	I1	I0	O	INIT=A8E6
Sel1	Sel0	A	B	Result	
0	0	0	0	0	6
0	0	0	1	1	
0	0	1	0	1	
0	0	1	1	0	
0	1	0	0	0	E
0	1	0	1	1	
0	1	1	0	1	
0	1	1	1	1	
1	0	0	0	0	8
1	0	0	1	0	
1	0	1	0	0	
1	0	1	1	1	
1	1	0	0	0	A
1	1	0	1	1	
1	1	1	0	0	
1	1	1	1	1	

 

```
def logicfunc(A, B, S0, S1):  
    if S1 == 0:  
        if S0 == 0:  
            return B  
        else:  
            return A&B  
    else:  
        if S0 == 0:  
            return A|B  
        else:  
            return A^B  
  
def Logic(n):  
    def logic(y):  
        return LUT4(logicfunc)  
    return braid(col(logic, n),  
                 joinargs=['I0', 'I1'],  
                 forkargs=['I2', 'I3'])
```

logic.py

mov.py

and.py

or.py

xor.py

Arith Unit

arith.py
add.py
sub.py
count.py

Condition Codes

blink.py

PLBs/LUTs

**Decode
Sequencer
Registers
Conditions
Logic
Arith
ALU
MUXes
Output**